



Faculty of Engineering & Technology Electrical & Computer Engineering

Department

ADVANCED DIGITAL SYSTEMS DESIGN ENCS3310

Course Project

Prepared by:

Hasan Hamed 1190496

Instructor: Dr. Abdallatif Abuissa

Section: 1

Date: 24/12/2021

1. Introduction & Background

The main goal of the project is to design an 8-bit signed comparator VHDL code which compares two numbers represented in two's complement representation structurally in two stages of complexity, first by using the ripple adder and negative, overflow and zero flags, and second by using the magnitude comparator and the sign bit of the two numbers, and finally, to test both circuits using effective test benches that reports if there is an error in the designs.

Table of Contents

1. Introduction & Background	II
2. Design philosophy.....	1
2.1. Stage 1	1
2.2. Stage 2	2
3.Results	3
3.1. Stage 1	3
3.2. Stage 2	4
4. Conclusion and Future works	5
5. Appendix.....	6
5.1. Flip Flop Code	6
5.2. Registers Code	7
5.3. Full Adder Code	8
5.4. Stage 1 Comparator Code.....	9
5.5. Stage 1 Top Level View Code.....	10
5.6. Stage 1 Test Bench.....	13
5.7. Stage 2 Comparator Code.....	16
5.8. Stage 2 Top Level View Code.....	18
5.9. Stage 2 Test Bench.....	21

Table of Figures

Figure 2.1: Block diagram of the 8-bit comparator.	1
Figure 2.2: 4-bit Signed comparator with flags.	1
Figure 2.3: 8-bit signed comparator using magnitude comparator and sign bit.....	2
Figure 3.1: Stage 1 simulation.	3
Figure 3.2: Stage 1 wrong circuit simulation.	3
Figure 3.3: Reporting error for wrong circuit of stage 1.	4
Figure 3.4: Stage 2 simulation.	4
Figure 3.5: Stage 2 wrong circuit simulation	4
Figure 3.6: Stage 2 wrong circuit simulation.	5

2. Design philosophy

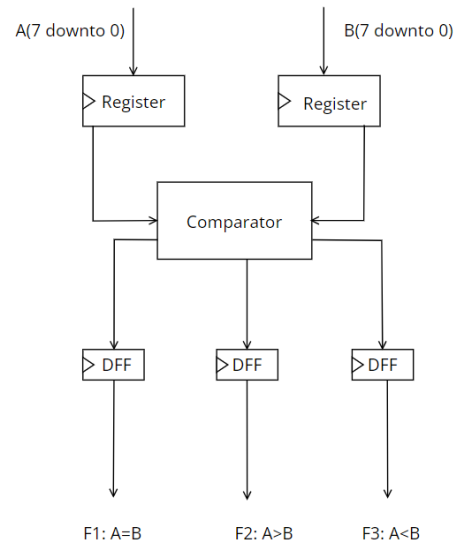


Figure 2.1: Block diagram of the 8-bit comparator.

As shown above in Figure 2.1, the comparator has two 8-bit inputs that are connected to the comparator from registers, and the outputs of the comparator is connected to output registers that give the output of the whole circuit.

2.1. Stage 1

In this stage, the signed comparator concept is by subtracting both numbers and determining the overflow, zero and negative flags as shown in Figure 2.2.

 


Figure 2.2: 4-bit Signed comparator with flags.

The 8-bit comparator will be designed by cascading this 4-bit comparator with another 4-bit comparator and then, the flags will be given by:

$$V = C(7) \text{ XOR } C(6)$$

$$N = S7$$

$$Z = \text{NOR}(S0 \text{ to } S7)$$

Using the three flags the three outputs can be easily determined by using those important rules about comparing in computer organization:

$$A=B \text{ when } Z=1$$

$$A>B \text{ when } Z=0 \text{ and } N=V$$

$$A<B \text{ when } N \neq V$$

Using that information, the outputs are given by:

$$F1 = Z$$

$$F2 = (N \text{ XNOR } V) \text{ AND } Z'$$

$$F3 = N \text{ XNOR } V$$

Latency = longest path = 2 inverter + (14*8) FA + 12 XOR + 9 XNOR + 2 inverters + 7 AND = 144 ns.

2.2. Stage 2

In this stage, the signed comparator was designed by comparing the magnitude of the 7 least significant bits of both numbers using magnitude comparator, and then using the sign bit and the output of the magnitude comparator to determine the output of the signed comparator.

F1 is generated by the equality circuit which is:

$$F1 = \text{AND } e(0 \text{ to } 7)$$

And e is given by:

$$e(0 \text{ to } 7) = A(0 \text{ to } 7) \text{ XNOR } B(0 \text{ to } 7)$$

Which means that both numbers are equal if every bit of each number is the same.

And having the equality output, the circuit design will become as shown in Figure 2.3.

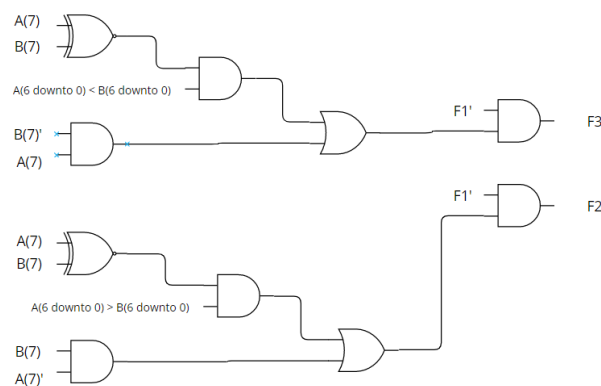


Figure 2.3: 8-bit signed comparator using magnitude comparator and sign bit.

A will be greater than B if both have the same sign and the magnitude of the least significant bits of A are greater than B and they are not equal or if the sign of A was positive and B is negative and they are not equal.

B will be greater than A if both have the same sign and the magnitude of the least significant bits of B are greater than A and they are not equal or if the sign of B was positive and A is negative and they are not equal.

Total latency = $2+14+7+7+7=37$ ns.

3.Results

3.1. Stage 1

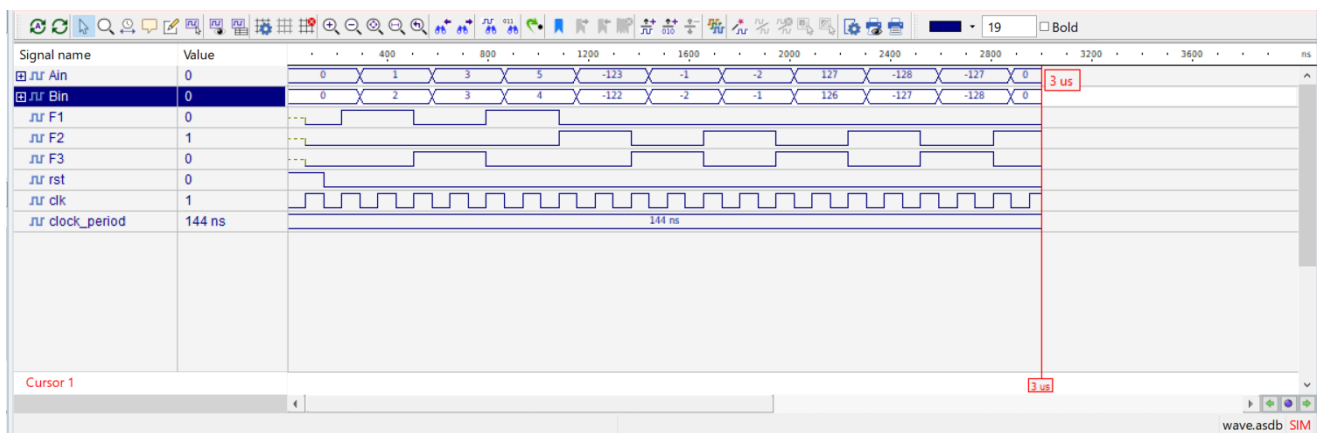


Figure 3.1: Stage 1 simulation.

As shown in Figure 3.1, results are correct for comparing both negative and positive numbers and large and small numbers, F1 when $A=B$ and F2 when $A>B$ and F3 when $A<B$. There is a 1 clock delay because inputs and outputs are connected to registers.

The design is also capable of detecting any error in the circuit using asserts as shown in Figure 3.2 and 3.3.

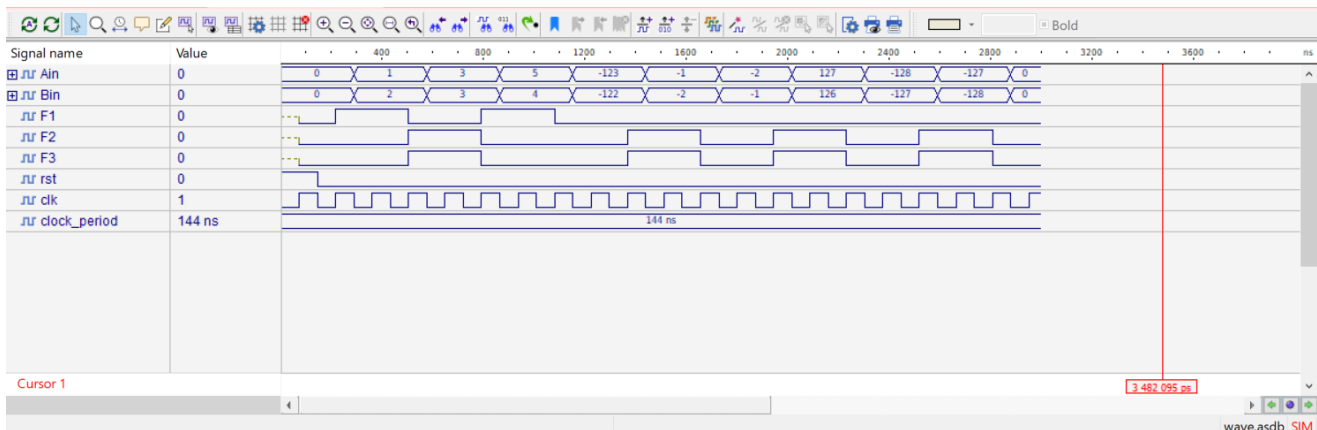


Figure 3.2: Stage 1 wrong circuit simulation.

```

o # EXECUTION:: ERROR : Faliure
o # EXECUTION:: Time: 1152 ns, Iteration: 0, Instance: /tb, Process: Verification.
o # EXECUTION:: ERROR : Faliure
o # EXECUTION:: Time: 1440 ns, Iteration: 0, Instance: /tb, Process: Verification.
o # EXECUTION:: ERROR : Faliure
o # EXECUTION:: Time: 1728 ns, Iteration: 0, Instance: /tb, Process: Verification.
o # KERNEL: stopped at time: 2 us
o run 1000 ns
o # EXECUTION:: ERROR : Faliure
o # EXECUTION:: Time: 2016 ns, Iteration: 0, Instance: /tb, Process: Verification.
o # EXECUTION:: ERROR : Faliure
o # EXECUTION:: Time: 2304 ns, Iteration: 0, Instance: /tb, Process: Verification.
o # EXECUTION:: ERROR : Faliure
o # EXECUTION:: Time: 2592 ns, Iteration: 0, Instance: /tb, Process: Verification.
o # EXECUTION:: ERROR : Faliure
o # EXECUTION:: Time: 2880 ns, Iteration: 0, Instance: /tb, Process: Verification.
o # KERNEL: stopped at time: 3 us

```

Figure 3.3: Reporting error for wrong circuit of stage 1.

3.2. Stage 2



Figure 3.4: Stage 2 simulation.

As shown in Figure 3.4, results are correct for comparing both negative and positive numbers and large and small numbers, F1 when $A=B$ and F2 when $A>B$ and F3 when $A<B$. There is a 1 clock delay because inputs and outputs are connected to registers.

The design is also capable of detecting any error in the circuit using asserts as shown in Figure 3.5 and 3.6.

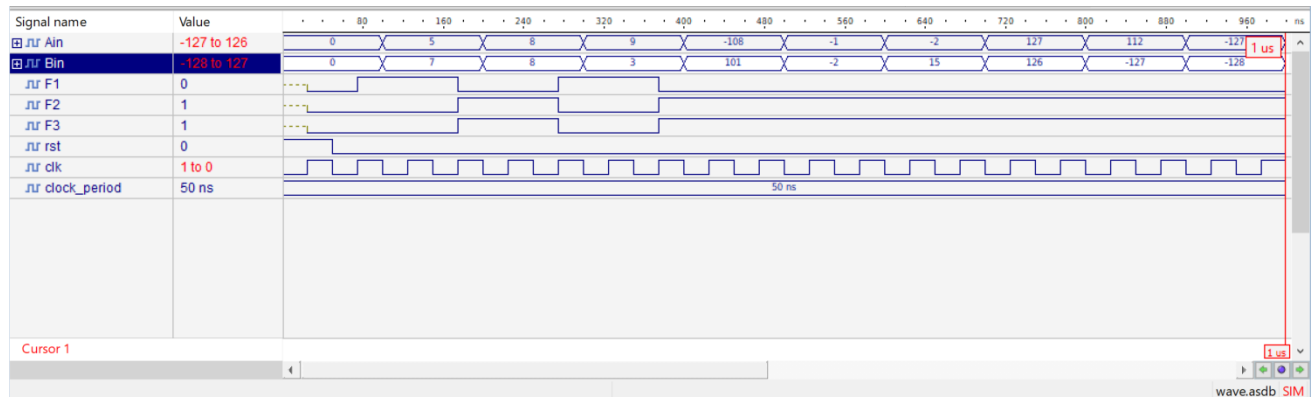


Figure 3.5: Stage 2 wrong circuit simulation

```

- - - - -
◦ # EXECUTION:: ERROR : Failure
◦ # EXECUTION:: Time: 200 ns, Iteration: 0, Instance: /tb, Process: Verification.
◦ # EXECUTION:: ERROR : Failure
◦ # EXECUTION:: Time: 400 ns, Iteration: 0, Instance: /tb, Process: Verification.
◦ # EXECUTION:: ERROR : Failure
◦ # EXECUTION:: Time: 500 ns, Iteration: 0, Instance: /tb, Process: Verification.
◦ # EXECUTION:: ERROR : Failure
◦ # EXECUTION:: Time: 600 ns, Iteration: 0, Instance: /tb, Process: Verification.
◦ # EXECUTION:: ERROR : Failure
◦ # EXECUTION:: Time: 700 ns, Iteration: 0, Instance: /tb, Process: Verification.
◦ # EXECUTION:: ERROR : Failure
◦ # EXECUTION:: Time: 800 ns, Iteration: 0, Instance: /tb, Process: Verification.
◦ # EXECUTION:: ERROR : Failure
◦ # EXECUTION:: Time: 900 ns, Iteration: 0, Instance: /tb, Process: Verification.
◦ # EXECUTION:: ERROR : Failure

```

Figure 3.6: Stage 2 wrong circuit simulation.

4. Conclusion and Future works

In conclusion, both stages of the 8-bit signed comparator worked perfectly and results were correct after testing it using test benches with asserts that reports if there exist an error in the circuit as was shown. Stage 1 was designed in a generic form which means it can be updated to compare between any n-bits numbers but stage 2 wasn't designed in a generic form which it can be updated to work on any number of bits on the future.

The signed 8-bit comparator can be used on security purposes such as opening doors of banks with passwords using microcontrollers, the comparator purpose is to compare between the number put by the person who wish to enter and the password that was defined before and thus the door will open by the signal sent when both numbers are equal (F1).

F2 and F3 can be used in evil ways, such as if the input was more or less than the password a signal will be sent to speakers that will alarm the user that someone is trying to open the door and security dogs' cells will be opened to attack the thief.

5. Appendix

5.1. Flip Flop Code

--D-Flip Flop Design For Outputs

library ieee;

use ieee.std_logic_1164.all;

entity flipflop is

port(

 clock : in std_logic;

 enable : in std_logic;

 reset : in std_logic;

 data_in: in std_logic;

 data_out : out std_logic);

end flipflop;

architecture behavior of flipflop is

begin

reg: process(clock)

begin

 if rising_edge(clock) then

 if (reset = '1') then

 data_out <= '0';

 elsif (enable = '1') then

 data_out <= data_in;

 end if;

 end if;

end process;

end behavior;

5.2. Registers Code

```
--generic register for inputs
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity regn is
generic(N : integer:=8 );
port(
    clk      : in std_logic;
    ena      : in std_logic;
    rst : in std_logic;
    din      : in STD_LOGIC_VECTOR(N-1 downto 0);
    dout     : out STD_LOGIC_VECTOR(N-1 downto 0));
end regn;

architecture regn of regn is
begin

reg:  process(clk)
    begin

        if rising_edge(clk) then
            if (rst = '1' ) then
                dout<= (OTHERS=>'0');
            elsif (ena ='1') then
                dout <= din;
            end if;
        end if;

    end process;

end regn;
```

5.3. Full Adder Code

--Designing FA to creat Ripple Adder

LIBRARY IEEE;

USE IEEE.STD_LOGIC_1164.ALL;

USE IEEE.NUMERIC_STD.ALL;

ENTITY FA IS

PORT (A : IN STD_LOGIC;

B : IN STD_LOGIC;

Cin : IN STD_LOGIC;

S : OUT STD_LOGIC;

Cout : OUT STD_LOGIC);

END FA;

ARCHITECTURE Behavioral OF FA IS

SIGNAL st,ct:std_logic;

BEGIN

ct<= ((B AND Cin) OR (A AND Cin) OR (A AND B)) AFTER 14 NS;

st<= (A XOR B XOR Cin) AFTER 12 NS;

S<= st ;

Cout<= ct ;

END Behavioral;

5.4. Stage 1 Comparator Code

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY comparator IS
  GENERIC(N: INTEGER := 8);
  PORT(
    a: IN STD_LOGIC_VECTOR(N-1 DOWNT0 0);
    b: IN STD_LOGIC_VECTOR(N-1 DOWNT0 0);
    f1, f2, f3: OUT STD_LOGIC
  );
END comparator;

ARCHITECTURE synth OF comparator IS
  SIGNAL S: STD_LOGIC_VECTOR(N-1 DOWNT0 0);           --Sum Signal
  SIGNAL notB: STD_LOGIC_VECTOR(N-1 DOWNT0 0);        --Inverting B to
  calculate 2's Complement
  SIGNAL t: STD_LOGIC_VECTOR(N DOWNT0 0);             -- Carry out of
  every adder
  SIGNAL z_flag, v_flag, n_flag: STD_LOGIC;

  COMPONENT FA IS
    PORT ( A : IN STD_LOGIC;
           B : IN STD_LOGIC;
           Cin : IN STD_LOGIC;
           S : OUT STD_LOGIC;
           Cout : OUT STD_LOGIC);
  END COMPONENT;

  BEGIN

    notB<= NOT(b) AFTER 2 NS;
    --Inverting B
    t(0) <= '1';
    -- Adding 1 after taking 1's complement of B to calculate 2's complement

    subtractor: FOR i IN 0 TO N-1 GENERATE-- Ripple Carry Adder
    BEGIN
      FA_X: FA PORT MAP( A => a(i), B=> notB(i), Cin =>t(i), S=>S(i), Cout=>t(i+1) );
      --Connecting Adders
    END GENERATE;
    z_flag <= NOT (S(0) OR S(1) OR S(2) OR S(3) OR S(4) OR S(5) OR S(6) OR S(7)) AFTER 9 NS;
    --Zero falg generation
    v_flag <= t(8) XOR t(7) AFTER 12 NS;                --Overflow flag generation
    n_flag <= S(7);                                     -- Negative flag generation
```

```

f3 <= n_flag XOR v_flag AFTER 12 NS;                                --A<B
using above flags
f2 <= (n_flag XNOR v_flag) and (NOT z_flag) AFTER 18 NS;            -- A>B using same flags
f1 <= z_flag ;
    -- A=B using zero flag

```

END synth;

5.5. Stage 1 Top Level View Code

--Top View Design to make testbench creation and simulating easier

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity top is

generic (

N : integer := 8

);

Port (Ain : in STD_LOGIC_VECTOR(N-1 downto 0);

Bin : in STD_LOGIC_VECTOR(N-1 downto 0);

F1_reg, F2_reg, F3_reg : out STD_LOGIC;

rst: in STD_LOGIC;

clk: in STD_LOGIC

);

end top;

architecture Behavioral of top is

signal Aout, Bout: STD_LOGIC_VECTOR(N-1 downto 0);

signal en_A, en_B, en_out: STD_LOGIC;

signal F1, F2, F3: STD_LOGIC;

component regn is

generic(N : integer:=8);

port(

clk : in std_logic;

ena : in std_logic;

rst : in std_logic;

din : in STD_LOGIC_VECTOR(N-1 downto 0);

dout : out STD_LOGIC_VECTOR(N-1 downto 0));

end component;

component flipflop is

port(

clk : in std_logic;

ena : in std_logic;

```

        rst : in std_logic;
        din   : in std_logic;
        dout  : out std_logic);
end component;

component comparator is
generic(N: integer := 8);
port(
    a: in STD_LOGIC_VECTOR(N-1 downto 0);
    b: in STD_LOGIC_VECTOR(N-1 downto 0);
    f1, f2, f3: out STD_LOGIC
);
end component;
begin

en_A<= '1';
en_B<= '1';
en_out<= '1';

Reg_A: regn
    generic map (N=> N)
    port map(
        clk=> clk,
        ena=> en_A,
        rst => rst,
        din=> Ain,
        dout=> Aout
    );

Reg_B: regn
    generic map (N=> N)
    port map(
        clk=> clk,
        ena=> en_B,
        rst => rst,
        din=> Bin,
        dout=> Bout
    );

FF_F1: flipflop
    port map(
        clk=> clk,
        ena=> en_out,
        rst => rst,
        din=> F1,

```

```

        dout=> F1_reg
    );

FF_F2: flipflop
    port map(
        clk=> clk,
        ena=> en_out,
        rst => rst,
        din=> F2,
        dout=> F2_reg
    );

FF_F3: flipflop
    port map(
        clk=> clk,
        ena=> en_out,
        rst => rst,
        din=> F3,
        dout=> F3_reg
    );

Comp_1: comparator
    generic map( N => N)
    port map(
        a=> Aout,
        b => Bout,
        f1 => F1,
        f2 => F2,
        f3 => F3
    );
end Behavioral;

```

5.6. Stage 1 Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.all;
ENTITY tb IS
END tb;

ARCHITECTURE behavioral OF tb IS
--Component Declaration for the Unit Under Test (UUT)
component top is
    generic (
        N      : integer := 8
    );
    Port ( Ain : in  STD_LOGIC_VECTOR(N-1 downto 0);
          Bin : in  STD_LOGIC_VECTOR(N-1 downto 0);

          F1_reg, F2_reg, F3_reg : out STD_LOGIC;
          rst: in STD_LOGIC;
          clk: in STD_LOGIC

    );
end component;

constant N: integer := 8;

SIGNAL Ain : STD_LOGIC_VECTOR (N-1 DOWNT0 0);
SIGNAL Bin : STD_LOGIC_VECTOR (N-1 DOWNT0 0);
SIGNAL F1, F2, F3 : STD_LOGIC;
SIGNAL rst: STD_LOGIC;
--Clock generation-----
SIGNAL clk:STD_LOGIC;
SIGNAL clock_period:time :=144ns; --period of clock

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    UUT: top
        generic map (N=> N)
        PORT MAP(
            clk => clk,
            rst => rst,
            Ain=> Ain,
            Bin=> Bin,
            F1_reg=> F1,
```



```

F2_reg=> F2,
F3_reg=>F3
);
--Making Clock
clock_process :process
begin
    clk <= '0';
    wait for clock_period/2;
    clk <= '1';
    wait for clock_period/2;
end process;
-- Test cases
Testing: process
begin
    Ain<= (others => '0');
    Bin<= (others => '0');
    rst<= '1';

    wait for clock_period;
rst<= '0';

    wait for clock_period;
    Ain<= x"01";
    Bin<= x"02";
    wait for 2*clock_period;
    Ain<= x"03";
    Bin<= x"03";
    wait for 2*clock_period;
    Ain<= x"05";
    Bin<= x"04";
    wait for 2*clock_period;
    Ain<= x"85";
    Bin<= x"86";
    wait for 2*clock_period;
    Ain<= x"FF";
    Bin<= x"FE";
    wait for 2*clock_period;
    Ain<= x"FE";
    Bin<= x"FF";
    wait for 2*clock_period;
    Ain<= x"7F";
    Bin<= x"7E";
    wait for 2*clock_period;
    Ain<= x"80";
    Bin<= x"81";
    wait for 2*clock_period;

```

```

Ain<= x"81";
Bin<= x"80";
wait for 2*clock_period;
Ain<= x"00";
Bin<= x"00";
wait for 2*clock_period;

```

```

        wait;
    end process;

```

```

-----
-- verifier
Verification: process
    variable error_status : boolean := true;
begin
    wait on Ain;
    wait for 2*clock_period;
    if ( (signed(Ain) = signed(Bin) and F1 = '1' and F2 = '0' and F3 = '0') or
        (signed(Ain) > signed(Bin) and F1 = '0' and F2 = '1' and F3 = '0') or
        (signed(Ain) < signed(Bin) and F1 = '0' and F2 = '0' and F3 = '1'))
    then
        error_status := false;
    else
        error_status := true ;
    end if;

-- error reporting
    assert not error_status
    report "Faliure"
    severity error ;
end process;

END;

```

5.7. Stage 2 Comparator Code

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY comparator IS
GENERIC(N: INTEGER := 8);
PORT(
    a: IN STD_LOGIC_VECTOR(N-1 DOWNT0 0);
    b: IN STD_LOGIC_VECTOR(N-1 DOWNT0 0);
    f1, f2, f3: OUT STD_LOGIC
);
END comparator;
ARCHITECTURE synth OF comparator IS
SIGNAL e: STD_LOGIC_VECTOR(N-1 DOWNT0 0);
SIGNAL agreat, aless: STD_LOGIC;                                -- Signals shown in Circuit in
Report                                                                    Report
SIGNAL great, less: STD_LOGIC_VECTOR (6 DOWNT0 0);    --Magnitude Comparator(long circuit)
Signals
SIGNAL not_a,not_b : STD_LOGIC_VECTOR (7 DOWNT0 0); --Inverters
SIGNAL f1_temp: STD_LOGIC;
SIGNAL n1,n2,n3,n4,n5,n6,n7,n8,n9: STD_LOGIC;          --Circuit in Report Signals
BEGIN

    e_gen: FOR i IN N-1 DOWNT0 0 GENERATE
        e(i)<= a(i) XNOR b(i) AFTER 12 ns;
    END GENERATE;

    f1_temp <= e(0) AND e(1) AND e(2) AND e(3) AND e(4) AND e(5) AND e(6) AND e(7)
AFTER 7 ns;                                --A=B
    f1<= f1_temp;

    not_a <= NOT a AFTER 2 ns;
    not_b <= NOT b AFTER 2 ns;

    great(6) <= a(6) and not_b(6) after 7 ns;
    great(5) <= e(6) and a(5) and not_b(5) after 7 ns;
    great(4) <= e(6) and e(5) and a(4) and not_b(4) after 7 ns;
    great(3) <= e(6) and e(5) and e(4) and a(3) and not_b(3) after 7 ns;
    great(2) <= e(6) and e(5) and e(4) and e(3) and a(2) and not_b(2) after 7 ns;
    great(1) <= e(6) and e(5) and e(4) and e(3) and e(2) and a(1) and not_b(1) after 7 ns;
    great(0) <= e(6) and e(5) and e(4) and e(3) and e(2) and e(1) and a(0) and not_b(0) after 7 ns;
    agreat <= great(6) or great(5) or great(4) or great(3) or great(2) or great(1) or great(0) after 7 ns;    --A>B

    less(6) <= not_a(6) and b(6) after 7 ns;
    less(5) <= e(6) and not_a(5) and b(5) after 7 ns;
```

```

less(4) <= e(6) and e(5) and not_a(4) and b(4) after 7 ns;
less(3) <= e(6) and e(5) and e(4) and not_a(3) and b(3) after 7 ns;
less(2) <= e(6) and e(5) and e(4) and e(3) and not_a(2) and b(2) after 7 ns;
less(1) <= e(6) and e(5) and e(4) and e(3) and e(2) and not_a(1) and b(1) after 7 ns;
less(0) <= e(6) and e(5) and e(4) and e(3) and e(2) and e(1) and not_a(0) and b(0) after 7 ns;
aless <= less(6) or less(5) or less(4) or less(3) or less(2) or less(1) or less(0) after 7 ns;
--A<B

```

```

n1 <= a(7) XNOR b(7) AFTER 9 ns;
n2 <= not_a(7) AND b(7) AFTER 7 ns;
n3 <= not_b(7) AND a(7) AFTER 7 ns;
n4 <= a(7) XNOR b(7) AFTER 9 ns;
n5 <= n4 AND aless AFTER 7 ns;
comparator signals as shown in Report
n6 <= n1 AND agreat AFTER 7 ns;
n7 <= n6 OR n2 AFTER 7 ns;
n8 <= n3 OR n5 AFTER 7 ns;
n9 <= not f1_temp after 2 ns;
--Signed

```

```

f2 <= n9 AND n7 AFTER 7 ns;
f3 <= n8 AND n9 AFTER 7 ns;
--Outputs

```

```

end synth;

```

5.8. Stage 2 Top Level View Code

--This file has all the components connected using port map so that the simulation of the testbench will be much easier

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY top IS
    GENERIC (
        N      : integer := 8
    );
    PORT ( Ain : IN  STD_LOGIC_VECTOR(N-1 DOWNT0 0);
          Bin : IN  STD_LOGIC_VECTOR(N-1 DOWNT0 0);

          F1_reg, F2_reg, F3_reg : out STD_LOGIC;
          rst: in STD_LOGIC;
          clk: in STD_LOGIC

    );
end top;
```

```
architecture Behavioral of top is
    signal Aout, Bout: STD_LOGIC_VECTOR(N-1 downto 0);
    signal en_A, en_B, en_out: std_logic;
    signal F1, F2, F3: std_logic;
```

```
component regn is
    generic(N : integer:=8 );
    port(
        clk      : in std_logic;
        ena      : in std_logic;
        rst : in std_logic;
        din      : in STD_LOGIC_VECTOR(N-1 downto 0);
        dout     : out STD_LOGIC_VECTOR(N-1 downto 0));
end component;
```

```
component flipflop is
    port(
        clock  : in std_logic;
        enable : in std_logic;
        reset  : in std_logic;
        data_in: in std_logic;
        data_out      : out std_logic);
end component;
```

```
component comparator is
    generic(N: integer := 8);
```

```

port(
    a: in STD_LOGIC_VECTOR(N-1 downto 0);
    b: in STD_LOGIC_VECTOR(N-1 downto 0);
    f1, f2, f3: out STD_LOGIC
);
end component;

```

```

begin

```

```

    en_A<= '1';
    en_B<= '1';
    en_out<= '1';

```

```

Register_A: regn

```

```

    generic map (N=> N)
    port map(
        clk=> clk,
        ena=> en_A,
        rst => rst,
        din=> Ain,
        dout=> Aout
    );

```

```

Register_B: regn

```

```

    generic map (N=> N)
    port map(
        clk=> clk,
        ena=> en_B,
        rst => rst,
        din=> Bin,
        dout=> Bout
    );

```

```

Comp_1: comparator

```

```

    generic map( N => N)
    port map(
        a=> Aout,
        b => Bout,

        f1 => F1,
        f2 => F2,
        f3 => F3
    );

```

```

Flip_Flop_F1: flipflop

```

```

    port map(

```

```

        clock=> clk,
        enable=> en_out,
        reset => rst,
        data_in=> F1,
        data_out=> F1_reg
    );

Flip_Flop_F2: flipflop
    port map(
        clock=> clk,
        enable=> en_out,
        reset => rst,
        data_in=> F2,
        data_out=> F2_reg
    );

Flip_Flop_F3: flipflop
    port map(
        clock=> clk,
        enable=> en_out,
        reset => rst,
        data_in=> F3,
        data_out=> F3_reg
    );

end Behavioral;
```

5.9. Stage 2 Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use ieee.numeric_std.all;
ENTITY tb IS
END tb;

ARCHITECTURE behavioral OF tb IS
--Component Declaration for the Unit Under Test (UUT)
component top is
    generic (
        N      : integer := 8
    );
    Port ( Ain : in  STD_LOGIC_VECTOR(N-1 downto 0);
          Bin : in  STD_LOGIC_VECTOR(N-1 downto 0);

          F1_reg, F2_reg, F3_reg : out STD_LOGIC;
          rst: in STD_LOGIC;
          clk: in STD_LOGIC
    );
end component;

constant N: integer := 8;

SIGNAL Ain : STD_LOGIC_VECTOR (N-1 DOWNT0 0);
SIGNAL Bin : STD_LOGIC_VECTOR (N-1 DOWNT0 0);
SIGNAL F1, F2, F3 : STD_LOGIC;
SIGNAL rst: STD_LOGIC;
--Clock generation-----
SIGNAL clk:STD_LOGIC;
SIGNAL clock_period:time :=50ns;

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    UUT: top
        generic map (N=> N)
        PORT MAP(
            clk => clk,
            rst => rst,
            Ain=> Ain,
            Bin=> Bin,
            F1_reg=> F1,
            F2_reg=> F2,
```



```

F3_reg=>F3
);

-- Clock process definitions
clock_process :process
begin
    clk <= '0';
    wait for clock_period/2;
    clk <= '1';
    wait for clock_period/2;
end process;
-- Test cases
Testing: process
begin
    Ain<= (others => '0');
    Bin<= (others => '0');
    rst<= '1';

    wait for clock_period;
rst<= '0';

    wait for clock_period;
    Ain<= x"05";
    Bin<= x"07";
    wait for 2*clock_period;
    Ain<= x"08";
    Bin<= x"08";
    wait for 2*clock_period;
    Ain<= x"09";
    Bin<= x"03";
    wait for 2*clock_period;
    Ain<= x"94";
    Bin<= x"65";
    wait for 2*clock_period;
    Ain<= x"FF";
    Bin<= x"FE";
    wait for 2*clock_period;
    Ain<= x"FE";
    Bin<= x"0F";
    wait for 2*clock_period;
    Ain<= x"7F";
    Bin<= x"7E";
    wait for 2*clock_period;
    Ain<= x"70";
    Bin<= x"81";
    wait for 2*clock_period;

```

```

Ain<= x"81";
Bin<= x"80";
wait for 2*clock_period;
Ain<= x"7E";
Bin<= x"7F";
wait for 2*clock_period;
Ain<= x"00";
Bin<= x"00";
wait for 2*clock_period;

```

```

        wait;
    end process;

```

```

-----
-- verifier

```

```

Verification: process

```

```

    variable error_status : boolean := true;

```

```

begin

```

```

    wait on Ain;

```

```

    wait for 2*clock_period;

```

```

    if ( (SIGNED(Ain) = SIGNED(Bin) and F1 = '1' and F2 = '0' and F3 = '0') or
        (SIGNED(Ain) > SIGNED(Bin) and F1 = '0' and F2 = '1' and F3 = '0') or
        (SIGNED(Ain) < SIGNED(Bin) and F1 = '0' and F2 = '0' and F3 = '1'))

```

```

    then

```

```

        error_status := false;

```

```

    else

```

```

        error_status := true ;

```

```

    end if;

```

```

-- error reporting

```

```

    assert not error_status

```

```

    report "Failure"

```

```

    severity error ;

```

```

end process;

```

```

END;

```